

ALU Design

CSE 306



Group – 5

Section – B1

Rolls: 1505076

1505079

1505080

1505081

1505086

1505089

1305065

Department of Computer Science and Engineering
Bangladesh University of Engineering and Technology


Problem Specification:

cin			Functions
cs2	cs1	Cs0	
0	0	0	Transfer A
0	1	0	Increment A
0	x	1	OR
1	0	0	Subtract with borrow
1	1	0	Subtract
1	x	1	AND


Arithmetic Part:

When $cs0 = 0$,


(a) Transfer A

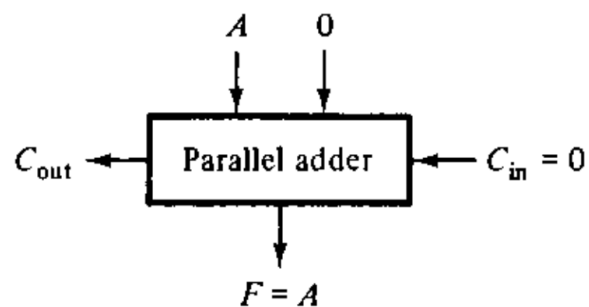

(b) Increment A

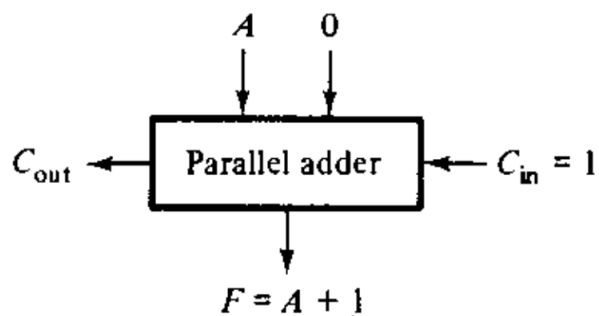

(c) Subtract with borrow

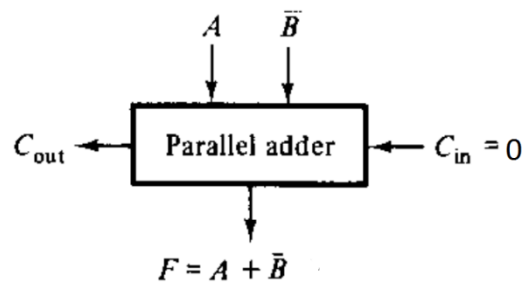

(d) Subtract

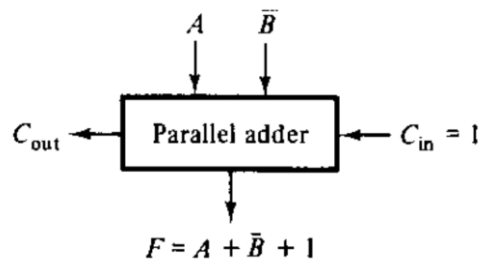


Table:

cs2	cs1	Y
0	0	0
0	1	0
1	0	B'
1	1	B'

$$Y_i = cs2.B_i' + cs2.cs1.B_i'$$

$$= cs2.B_i'$$

$$X_i = A_i$$

Logical Part:

When $cs_0 = 1$ logical part is activated and cs_1 is don't-care. We can force it to 0 by making $Cin = cs_0'.cs_1$. We also make every carry to next adder 0 in the same way.

Now,

cs_2	cs_1	cs_0	X_i	Y_i	Cin	Operation	Required Operation
0	X	1	A_i	0	0	$F_i = A_i$	OR
1	X	1	A_i	B_i'	0	$F_i = A_i \oplus B_i'$	AND

So when $cs_0 = 1$ and $cs_2 = 0$, we can OR B_i with A_i and the result will be $A+B$.

$$\therefore X_i = A_i + cs_2'.cs_0.B_i$$

Again when $cs_2 = 1$ and $cs_0 = 1$, we have to get AND operation where the output is equivalence.

$$F_i = A_i \oplus B_i' = A_i.B_i + A_i'.B_i'$$

Let us investigate the possibility of ORing each input A_i with some Boolean function K_i when $cs_2 = 1$ and $cs_0 = 1$.

$$F_i = X_i \oplus Y_i$$

$$= (A_i + K_i) \oplus B_i'$$

$$= A_i.B_i + K_i.B_i + A_i'.K_i'.B_i'$$

Taking $K_i = B_i'$, we get, $F_i = A_i.B_i + B_i'.B_i + A_i'.B_i.B_i' = A_i.B_i$, which is the required operation.

$$\text{So, finally } X_i = A_i + cs_2'.cs_0.B_i + cs_2.cs_0.B_i'$$

$$= A_i + cs_0.(cs_2'.B_i + cs_2.B_i')$$

$$= A_i + cs_0.(cs_2 \oplus B_i)$$

$$Y_i = cs_2.B_i'$$

$$Cin = cs_0'.cs_1$$

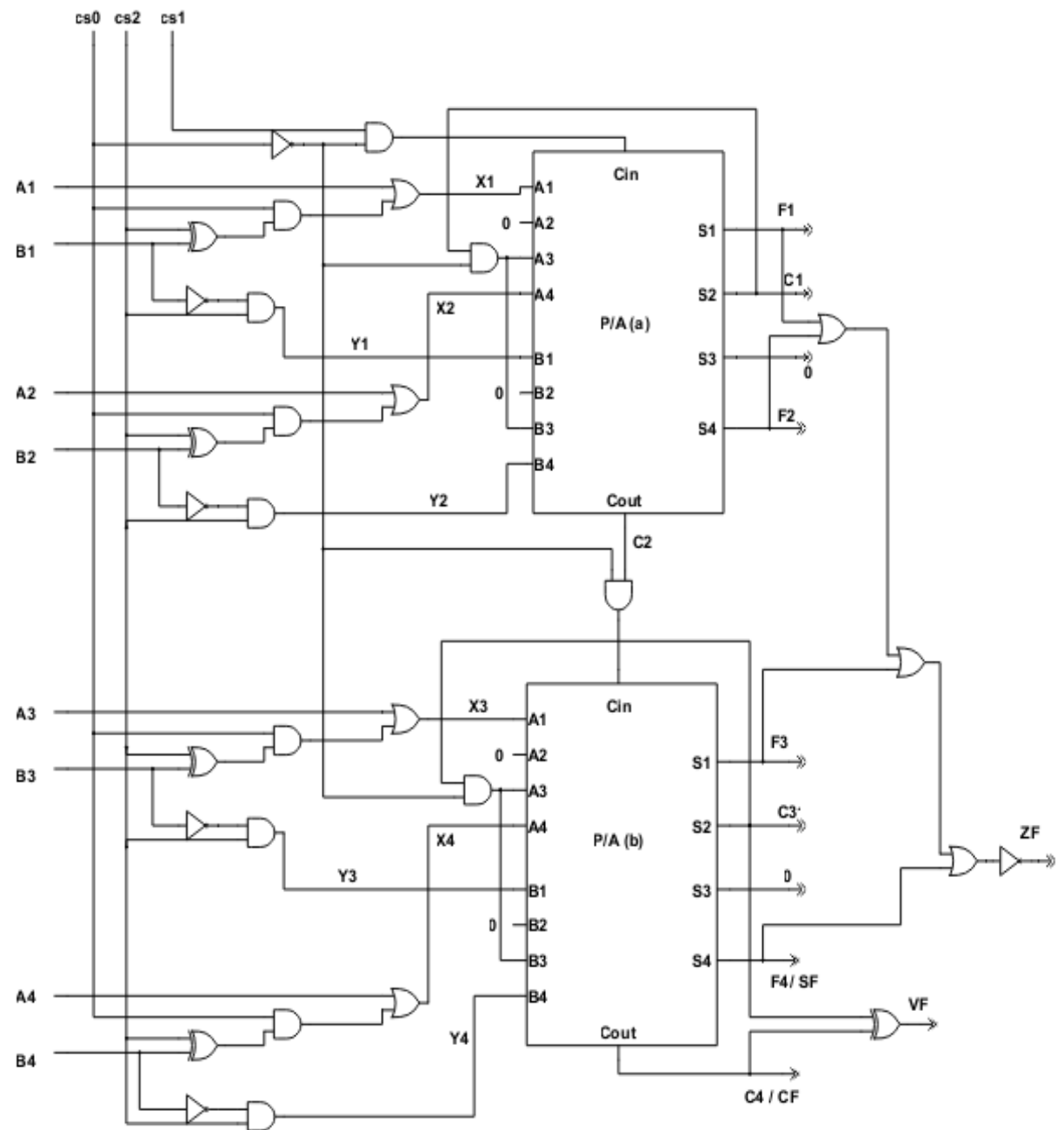


Fig : Design of 4-bit ALU